

CMR TECHNICAL CAMPUS

UGC AUTONOMOUS

B. Tech. II Sem Supply End Examinations, January-2024

Basic Electrical and Electronics Engineering

Common to ECE, AIML, CSM, CSC

Time: 3 Hours

Max. Marks: 60

Note

- This Question paper contains Part- A and Part- B.
- All the Questions in Part A are to be answered compulsorily.
- All Questions from Part B are to be answered with internal choice among them.

PART-A

10 X 01 = 10 Marks

	Marks	CO	BL
1. a State Kirchhoff's law.	1	CO1	L1
b Obtain expressions for the equivalent star network resistances for a given delta network.	1	CO1	L3
c The r.m.s. value of a sine wave is 100 A. Find its peak value.	1	CO2	L3
d How much r.m.s. current does a 300 W 200 V bulb take from the 200 V, 50 Hz power line?	1	CO2	L3
e State the condition for maximum efficiency in a transformer.	1	CO3	L2
f Express the torque equation of D.C. motor.	1	CO3	L2
g What is peak inverse voltage?	1	CO4	L2
h Sketch the bridge rectifier circuit.	1	CO4	L1
i What are the different configurations of BJT?	1	CO5	L2
j Show how α and β are related to each other.	1	CO5	L3

PART- B

5 X 10 = 50 Marks

	Marks	CO	BL
2 Demonstrate the nodal voltage method for solving networks. How are the nodal equations written?	10	CO1	L4
OR			
3 A resistance of 10 ohms is connected in series with a combination of two resistances arranged in parallel each of value 20 ohms. Determine the resistance R_3 which should be shunted across the parallel combination so that current drawn by the circuit is 1.5 A with applied voltage of 20 V	10	CO1	L3

- | | | | | |
|-----|---|----|-----|----|
| 4 | A circuit is made of two branches in parallel, one having a resistance of 10 ohms, in series with an inductive reactance of 20 ohms, the other having a resistance of 15 ohms in series with a capacitive reactance of 15 ohms. The supply voltage is 200 V. Find the total current, power and power factor | 10 | CO2 | L3 |
| OR | | | | |
| 5 | Analyse the current relationship and the voltage relationship in a 3-phase star connected system. Also derive the equation for power in such a system. | 10 | CO2 | L4 |
| 6 | Develop the equivalent circuit of a single phase transformer. | 10 | CO3 | L4 |
| OR | | | | |
| 7 | Describe the working of a three phase induction motor. What are its applications? | 10 | CO3 | L2 |
| 8 | Plot the V-I characteristic of zener diode and explain its operation. | 10 | CO4 | L2 |
| OR | | | | |
| 9 | Derive expressions for rectification efficiency, ripple factor, transformer utilisation factor and peak factor of a half wave rectifier with resistive load. | 10 | CO4 | L3 |
| 10 | With the help of V-I characteristics describe the working principle of an SCR. | 10 | CO5 | L2 |
| OR | | | | |
| 11. | Compare and contrast CE, CB and CC configurations of transistors. | 10 | CO5 | L4 |

CO : Course Outcomes

BL : Bloom's Taxonomy Levels

L 1 : Remembering

L 2 : Understanding

L 3 : Applying

L 4 : Analysing

L 5 : Evaluating

L 6 : Creating

CMR TECHNICAL CAMPUS
UGC AUTONOMOUS

B. Tech. I Semester Supply End Examinations, September-2023
Basic Electrical & Electronics Engg
Common to CSE, IT & CSD

Time: 3 Hours

Max. Marks: 60

Note

- This Question paper contains Part- A and Part- B.
- All the Questions in Part A are to be answered compulsorily.
- All Questions from Part B are to be answered with internal choice among them.

PART-A


10 X 01 = 10 Marks

	Marks	CO	BL
1. a Define KCL, KVL?	1	CO1	L2
b What are the different types of electrical elements?	1	CO1	L2
c Define Form factor and peak factor?	1	CO2	L2
d What is real power and reactive power?	1	CO2	L2
e What is principle of transformer?	1	CO3	L2
f Define Slip?	1	CO3	L2
g What is diode current equation?	1	CO4	L2
h What are the characteristics of Zener Diode?	1	CO4	L2
i What is SCR?	1	CO5	L2
j What is transistor?	1	CO5	L2

PART- B

5 X 10 = 50 Marks


	Marks	CO	BL
2. a For the given circuit, determine the current in 5Ω resistor?	5	CO1	L3

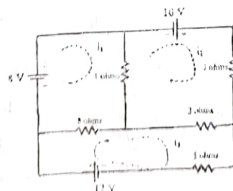

b Derive the equations for star to delta and delta to star transformation?	5	CO1	L4
OR			
3 a Using node voltage method to find the current in the 10Ω resistance of the following circuit shown in below figure	5	CO1	L3



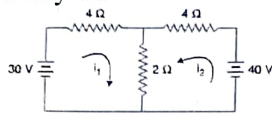- b Determine the current in all the branches of the network using analysis. loop



- 4 Derive the expression for RMS value, AVG value, Form factor and Peak factor of a sawtooth wave? 10 CO2 L4
- OR
- 5 a A 100 Ω resistor, 20 μ F capacitor and a 2H inductor are connected in series. At what frequency is the phase angle 45° . 5 CO2 L3
- b A wire carries a current, which is a combination of a d.c current of 10A and a sinusoidal current with a peak value of 10A. Determine RMS value of the resultant. 5 CO2 L3
- 6 What is principle of DC generator and With a neat diagram Explain the Construction of DC machine? 10 CO3 L2
- OR
- 7 a What is principle of transformer and derive its emf equation? 5 CO3 L2
- b Derive the torque equation of DC Motor? 5 CO3 L2
- 8 a Explain the operation of PN junction diode and draw its V-I characteristics? 5 CO4 L2
- b With a neat diagram explain the operation of Half wave rectifier? 5 CO4 L2
- OR
- 9 a Compare the characteristics of centre tapped transformer type and bridge type full wave Rectifiers. 5 CO4 L4
- b Define the terms dynamic resistance of a diode and Diffusion capacitance of a diode 5 CO4 L2
- 10 a Explain the construction and operation of SCR 5 CO5 L2
- b Compare CE, CB and CC characteristics of a BJT 5 CO5 L2
- OR
- 11 a Explain the construction and operation of CC amplifier? 5 CO5 L2
- b Explain the construction and operation of CE amplifier? 5 CO5 L2

CO : Course Outcomes

BL : Bloom's Taxonomy Levels L 1 : Remembering

L 2 : Understanding

L 3 : Applying

L 4 : Analysing

L 5 : Evaluating

L 6 : Creating

CMR TECHNICAL CAMPUS

UGC AUTONOMOUS

B. Tech. II Sem Supply End Examinations, January-2024

Basic Electrical Engineering

Department of ECE

Time: 3 Hours

Max. Marks: 70

Note

- This Question paper contains Part- A and Part- B.
- All the Questions in Part A are to be answered compulsorily.
- All Questions from Part B are to be answered with internal choice among them.

PART-A


10 X 02 = 20 Marks

	Marks	CO	BL
1. a Write the volt-ampere relations of R, L, C parameters.	2	CO1	L2
b State Thevenin's Theorem?	2	CO1	L1
c Define real and Reactive power?	2	CO2	L1
d Define form factor?	2	CO2	L1
e Draw No load phasor diagram of single-phase transformer.	2	CO3	L2
f What is an auto-transformer?	2	CO3	L2
g List the basic requirements to produce e.m.f.	2	CO4	L2
h What is the necessity of starter for DC motor?	2	CO4	L1
i Write the full forms of (i) MCB, (ii) MCCB and (iii) ELCB	2	CO5	L1
j What is the purpose of earthing?	2	CO5	L2

PART- B

5 X 10 = 50 Marks

	Marks	CO	BL
2. a State and explain Kirchoff's laws.	5	CO1	L2
b Determine the current flowing through the 10Ω resistor using Thevenin's theorem.	5	CO1	L5

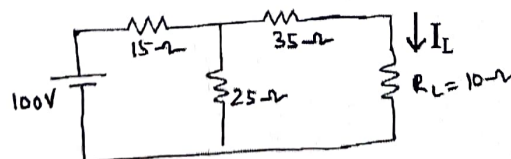

OR

3. a Discuss independent and dependent sources briefly?	5	CO1	L2
b Derive the transient DC response of series RL circuit?	5	CO1	L2

9

- | | | | | | |
|----|---|--|---|-----|----|
| 4 | a | Describe the generation of sinusoidal signal with neat sketch. | 5 | CO2 | L2 |
| | b | Obtain the phase relation between current & voltage when RC series circuit is connected across sinusoidal voltage. | 5 | CO2 | L2 |
| OR | | | | | |
| 5 | a | Explain the concept of Average value and RMS value. | 5 | CO2 | L2 |
| | b | Derive the relation between line and phase voltages and currents for a balanced STAR connected system. | 5 | CO2 | L2 |
| 6 | a | Explain operation of transformer on No load? | 5 | CO3 | L2 |
| | b | Explain various losses in single phase transformer. | 5 | CO3 | L2 |
| OR | | | | | |
| 7 | a | Develop equivalent circuit of 1-phase transformer? | 5 | CO3 | L2 |
| | b | Draw the connection diagrams of Y-Y, Y- Δ three-phase transformer connections. | 5 | CO3 | L2 |
| 8 | a | Explain in brief the functions of the following parts of a DC Machine (i) Field Poles (ii) Armature (iii) Brushes and (iv) Commutator. | 5 | CO4 | L2 |
| | b | Explain with sketches the constructional features of synchronous generator. | 5 | CO4 | L2 |
| OR | | | | | |
| 9 | a | Explain working principle of 3-phase induction motor. | 5 | CO4 | L2 |
| | b | Describe briefly torque-slip characteristics of induction motor. | 5 | CO4 | L2 |
| 10 | a | Explain construction and operation of MCB? | 5 | CO5 | L2 |
| | b | Discuss the important characteristics of batteries? | 5 | CO5 | L2 |
| OR | | | | | |
| 11 | a | Explain different types of wiring system. | 5 | CO5 | L2 |
| | b | Discuss the power factor improvement methods briefly. | 5 | CO5 | L2 |

CMR TECHNICAL CAMPUS

UGC AUTONOMOUS

B. Tech. I Semester Regular & Supply End Examinations, January-2024

Basic Electrical & Electronics Engineering

(Common to CSE, IT, CSIT & CSD)

Time: 3 Hours

Max. Marks: 60

Note

- i. This Question paper contains Part- A and Part- B.
- ii. All the Questions in Part A are to be answered compulsorily.
- iii. All Questions from Part B are to be answered with internal choice among them.

PART-A


10 X 01 = 10 Marks

		Marks	CO	BL
1	a	1M	CO1	L2
	b	1M	CO1	L1
	c	1M	CO2	L2
	d	1M	CO2	L1
	e	1M	CO3	L3
	f	1M	CO3	L2
	g	1M	CO4	L2
	h	1M	CO4	L2
	i	1M	CO5	L3
	j	1M	CO5	L1


PART- B

5 X 10 = 50 Marks

		Marks	CO	BL
2	a	3	CO1	L2
	b	7	CO1	L3
<p>Two resistances of 20 ohms and 30 ohms respectively are connected in parallel. These two parallel resistances are further connected in series with a resistance of 15 ohms. If the current through the 15 ohms resistance is 3A. Find</p> <p>(i) the voltage across the whole circuit</p> <p>(ii) the total power consumed</p>				
OR				
3	a	5	CO1	L5
	b	5	CO1	L3

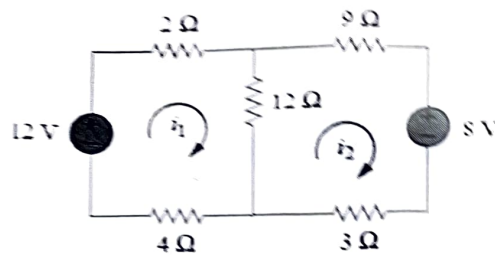

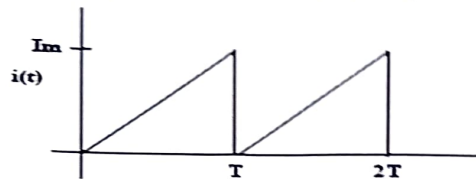- 4 a Define Average value, RMS value, Form factor & Peak factor. 3 CO2 L2
- b For the waveform shown in Figure below determine for each (i) the frequency (ii) the average value over half a cycle (iii) the RMS value (iv) the form factor (v) the peak factor. 7 CO2 L3



OR

- 5 a Explain the response of series RL circuit for a sinusoidal voltage source. 5 CO2 L1
- b Discuss the voltage and current relationship in Balanced star connection. 5 CO2 L3
- 6 a Develop an equation for induced e.m.f in a transformer winding in terms of flux and frequency. 5 CO3 L3
- b Describe various types of DC generators with their field and armature connections. 5 CO3 L4

OR

- 7 a With a neat circuit diagram explain the construction of DC motor. 5 CO3 L3
- b Explain working principle of three phase induction motor. 5 CO3 L1
- 8 a Explain the operation of diode and deduce its current equation. 5 CO4 L2
- b Discuss the operation of full wave rectifier with relevant waveforms. 5 CO4 L1

OR

- 9 a Write a short notes on; 3 CO4 L2
- (i) Transformer Utilisation Factor
- (ii) Peak Inverse Voltage
- b Explain the operation of zener diode with required circuit and characteristics. 7 CO4 L1
- 10 a Describe about Bipolar Junction Transistor? 5 CO5 L1
- b Explain the working of CB configuration of a BJT and draw its input, output characteristics. 5 CO5 L2

OR

- 11 a With neat sketch explain the constructional details of SCR. 5 CO5 L2
- b Compare the differences between CE, CB and CC configurations. 5 CO5 L4